

fesse

wve

wv


wv

Date of exam is :-2019-09-11

Name : _____ Group _____ Rno : _____

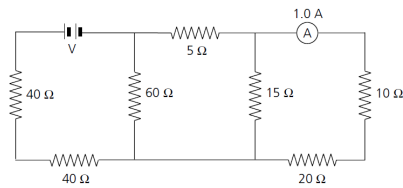1) solve the below question(2 marks)

***38 Figure 22.34 shows a complex circuit. Calculate the following values:
(a) total circuit resistance;
(b) voltage drop across the $60\ \Omega$ resistor.



Enter answer to the subjective question below